

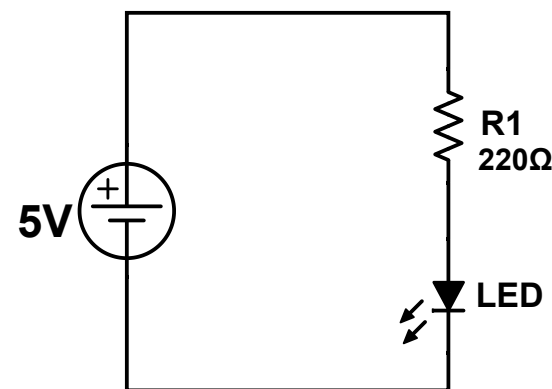


ELT1010 Circuits Workbook


Lesson 2

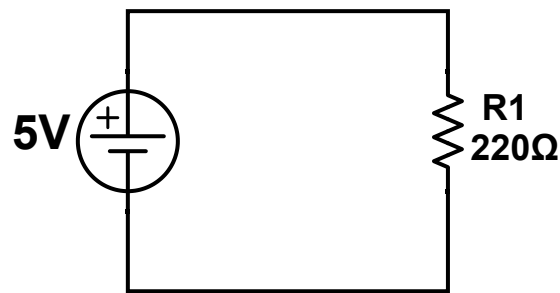


Lesson 3

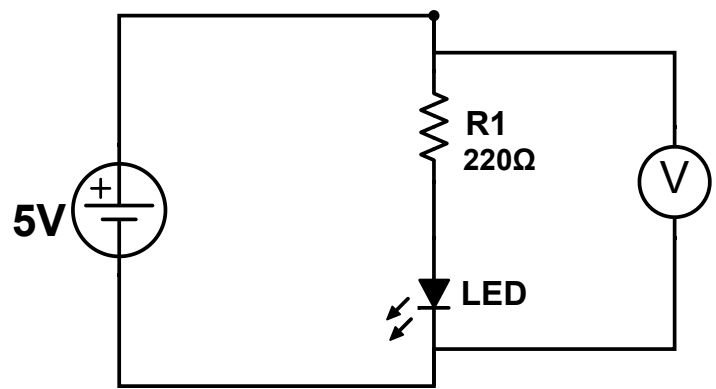

| | |
|------------------|--|
| V_{tot} | |
|------------------|--|

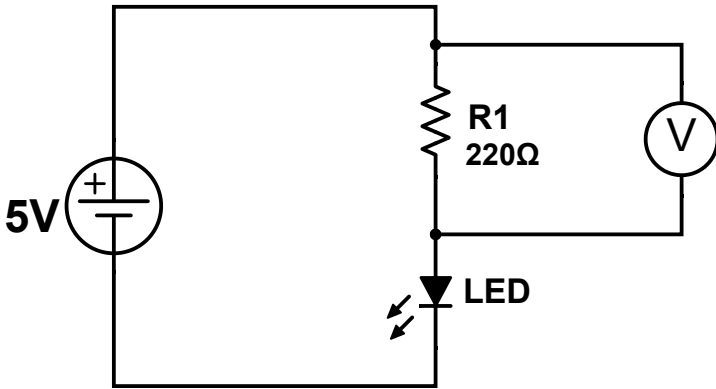


| | |
|----------|--|
| V_{R1} | |
|----------|--|

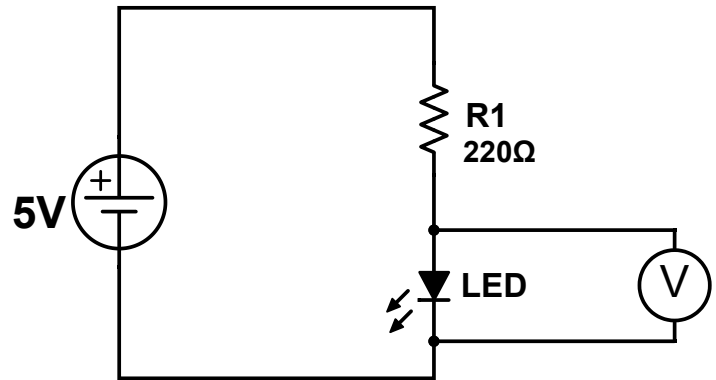


| | |
|------------------|--|
| V_{LED} | |
|------------------|--|

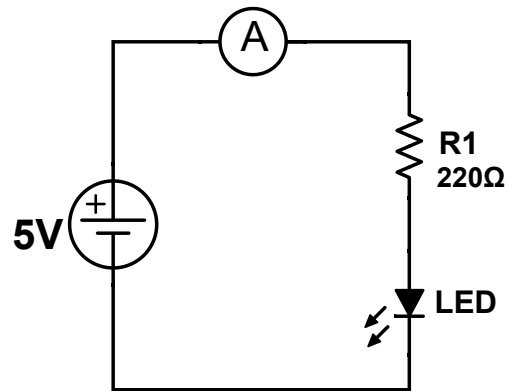What is the relationship between V_{R1} , V_{LED} , and V_{tot} ?



| | |
|-----------|--|
| I_{tot} | |
|-----------|--|

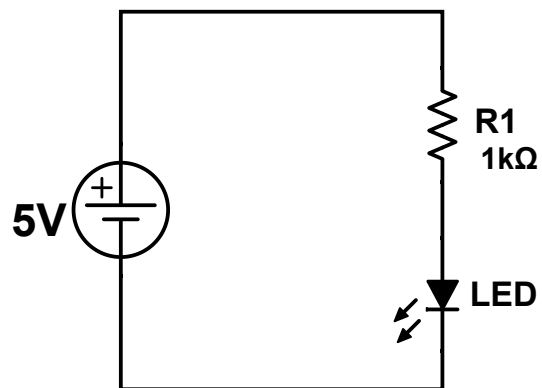


| | | | |
|----------|--|-----------|--|
| V_{R1} | | I_{tot} | |
|----------|--|-----------|--|


Ohm's Law: $I = V/R$

What current would we expect if $R1$ was $10k\Omega$?

Lesson 4

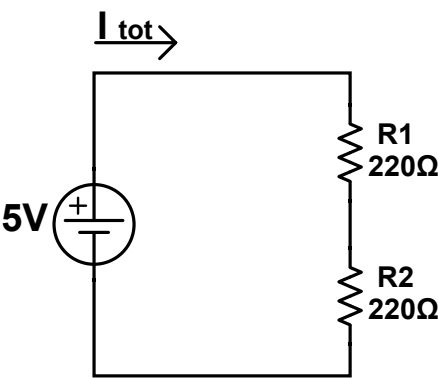


| | | | | | |
|-------------------|--|-------------------|--|-------------------|--|
| I_{tot} (meas.) | | R_{tot} (calc.) | | | |
| V_{R1} (meas.) | | V_{R2} (meas.) | | $V_{R1} + V_{R2}$ | |

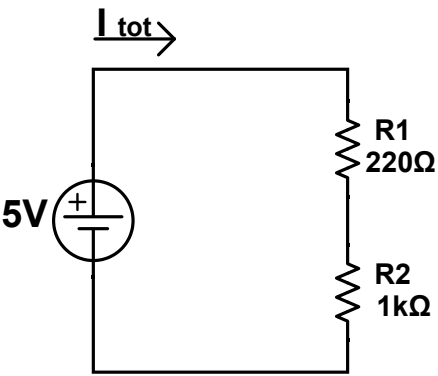


| | | | | | |
|-------------------|--|-------------------|--|-------------------|--|
| R_{tot} (calc.) | | I_{tot} (calc.) | | I_{tot} (meas.) | |
| V_{R1} (meas.) | | V_{R2} (meas.) | | $V_{R1} + V_{R2}$ | |

Lesson 5

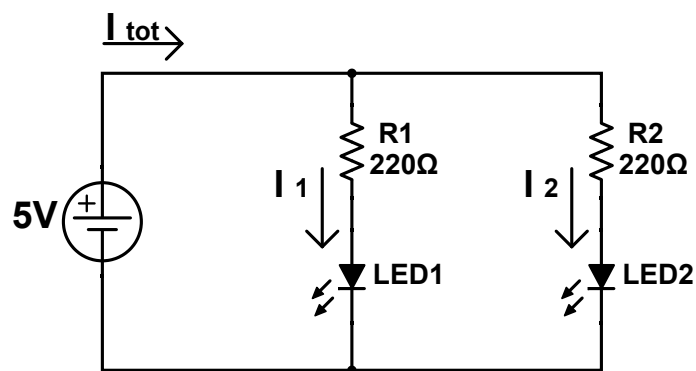


| | | | | | |
|-------------------|--|---------------|--|---------------|--|
| V_{R1} (meas.) | | I_1 (calc.) | | I_1 (meas.) | |
| V_{R2} (meas.) | | I_2 (calc.) | | I_2 (meas.) | |
| I_{tot} (meas.) | | | | | |

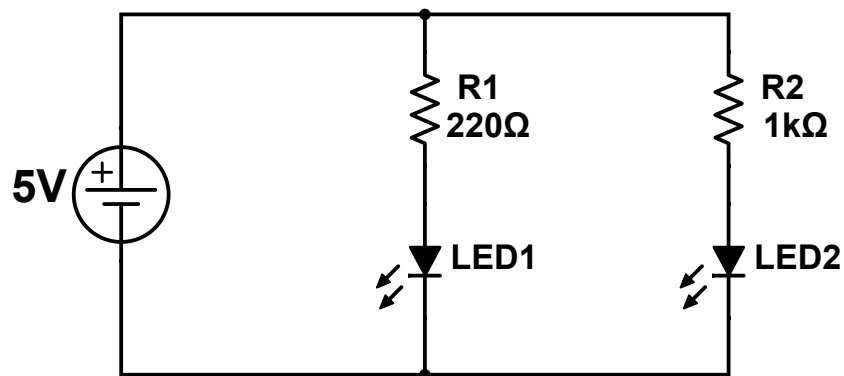What is the relationship between I_1 , I_2 , and I_{tot} ?





| | | | | | |
|-------------------|--|-------------------|--|---------------|--|
| V_{R1} (meas.) | | I_1 (calc.) | | I_1 (meas.) | |
| V_{R2} (meas.) | | I_2 (calc.) | | I_2 (meas.) | |
| I_{tot} (calc.) | | I_{tot} (meas.) | | | |


Lesson 6

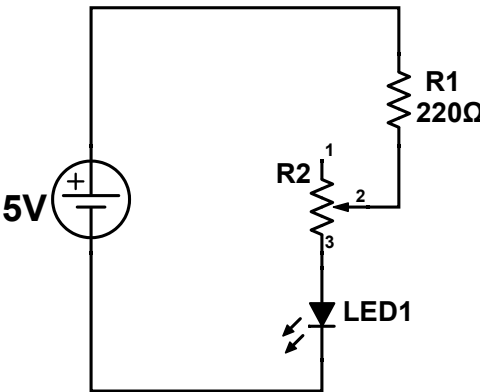


Lesson 7

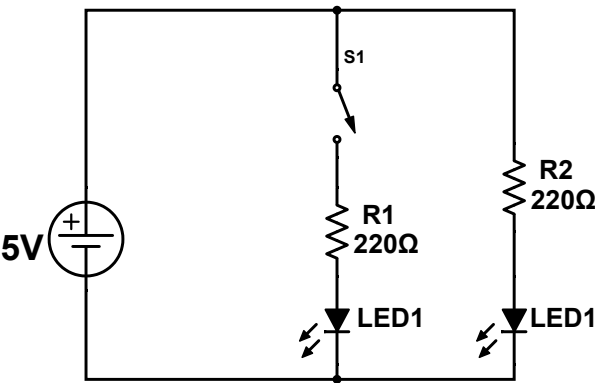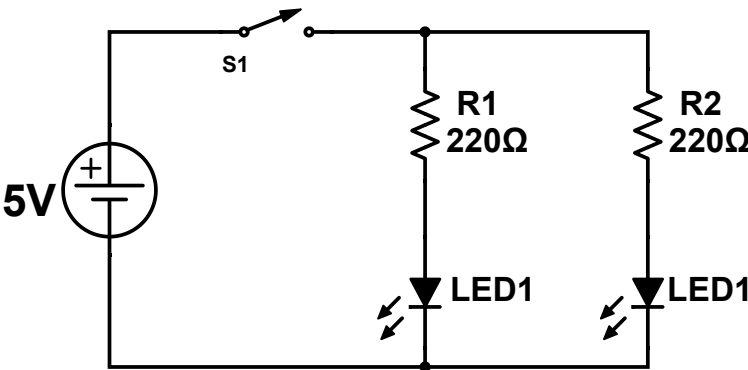

Lesson 8

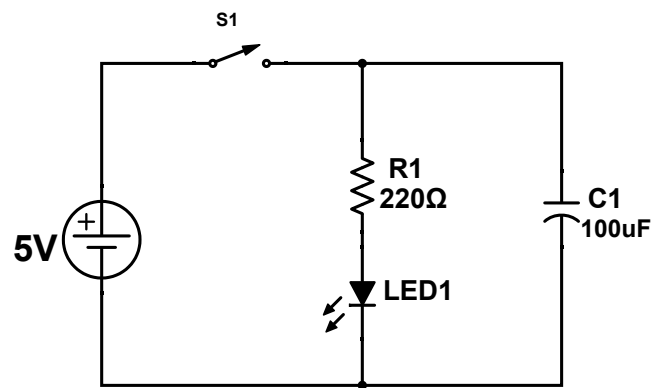

Lesson 9

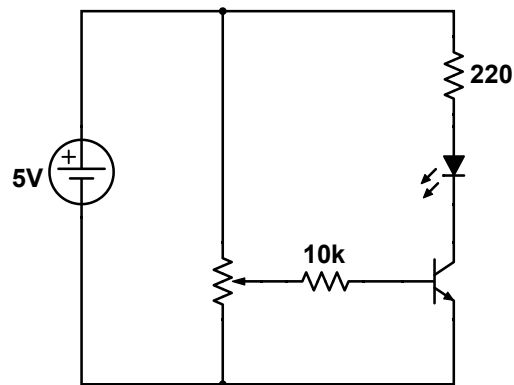

| | |
|-------------------------------------|--|
| V _{eb} to activate (meas.) | |
|-------------------------------------|--|